
 


Question 4-1:

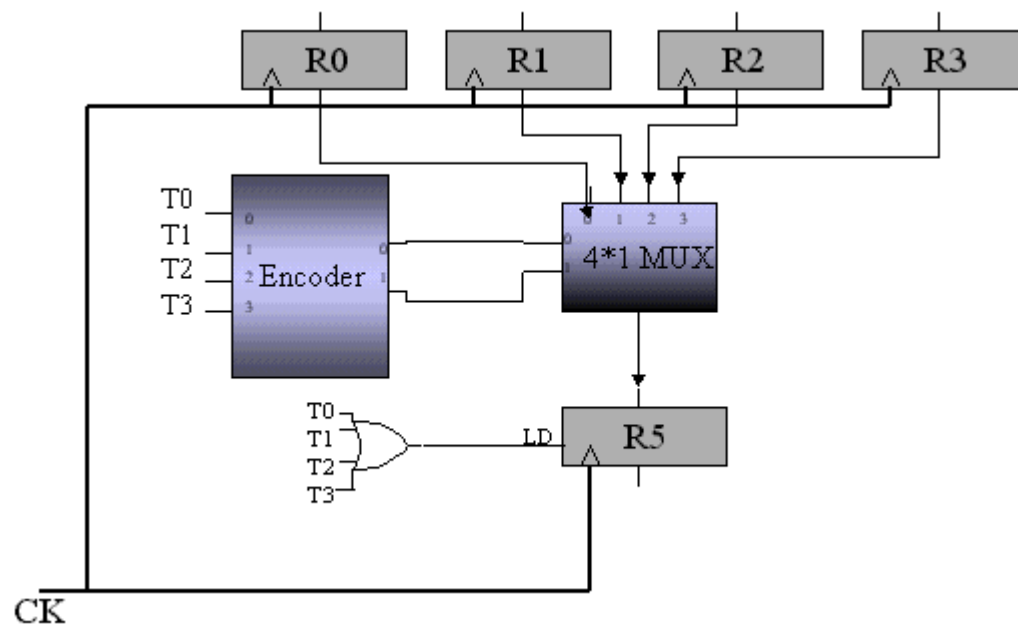

This RTL statement can happen provided that registers are of edge triggered type.¹

Question 4-2:



Question 4-3:


P: $R1 \leftarrow R2$

P'Q: $R1 \leftarrow R3$

¹ "Computer System Architecture" M. Morris Mano, page 97

Question 4-4:

In this question we use S1 S0 to select the source register (With S1 being HSB), and use S3 S2 to select among the four registers available (with S3 being the HSB).

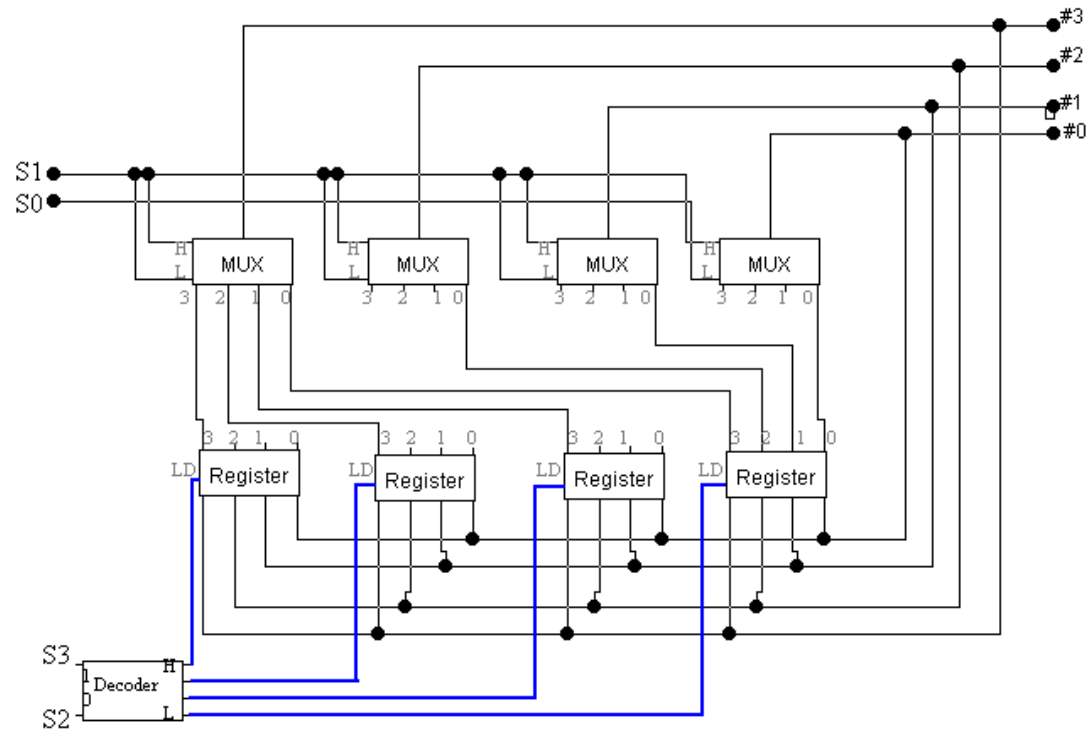**Question 4-5:**

a) $IR \leftarrow M[PC]$

We can't use the PC as an address to Memory, because Memory takes its address from AR Register.

We can write it as:

$AR \leftarrow PC$

$IR \leftarrow M[AR]$

b) $AC \leftarrow AC + TR$

There is no such access to AC except for INPR, DR and itself, so the correct form would be:

$DR \leftarrow TR$

$AC \leftarrow AC + DR$

c) $DR \leftarrow DR + AC$ (AC doesn't change):

This would change the value of AC to $AC + DR$. Also the Adder and Logic Unit should save its result in AC not in DR. The correct form would be:

$TR \leftarrow AC$

$AC \leftarrow AC + DR$

$DR \leftarrow AC$

$AC \leftarrow TR$

Question 4-6:

- a) 4 Selection Lines.
- b) 16x1 MUX's
- c) 32 MUX

Question 4-7:

- a) $R2 \leftarrow M[AR]$



This statement would transfer the contents of Memory word that has the address specified by AR into R2 register.

- b) $M[AR] \leftarrow R3$:


WRITE the value in register R3 into the Memory Word that has the address specified in AR.

- d) $R5 \leftarrow M[R5]$:


It will firstly READ the Memory Word specified by R5 and then transfer the value into the same register R5, this is mostly used in Indirect Addressing.

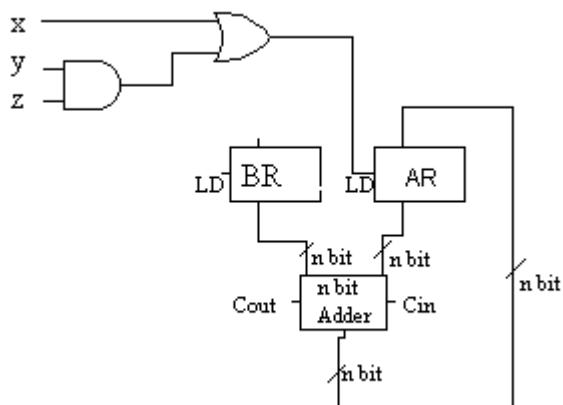 Question 4-8:**Question 4-9:**

Question 4-10:

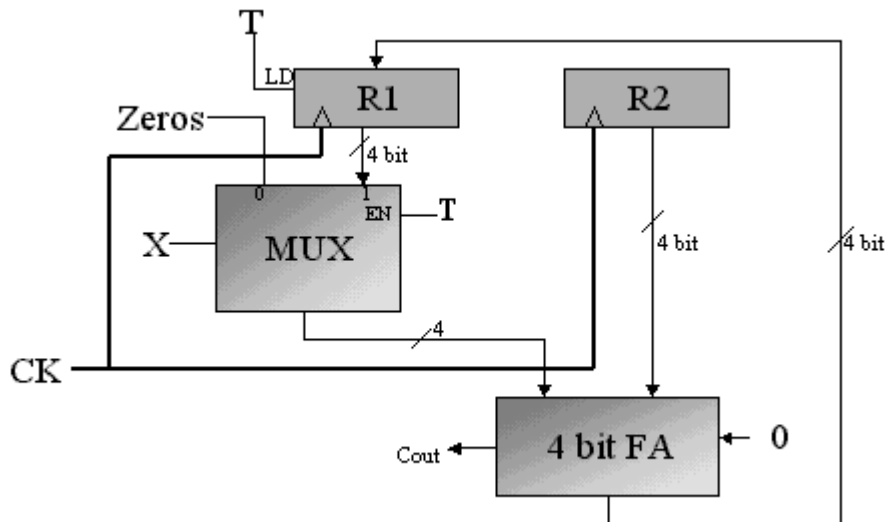


Question 4-11:

 


Question 4-12:

	S3	S2	S1	S0	C4	
A	1	1	0	1	0	7+6
B	0	0	0	1	1	8+9
C	0	1	0	0	1	12-8
D	1	0	1	1	0	5-10
E	1	1	1	1	0	-1


Question 4-13:

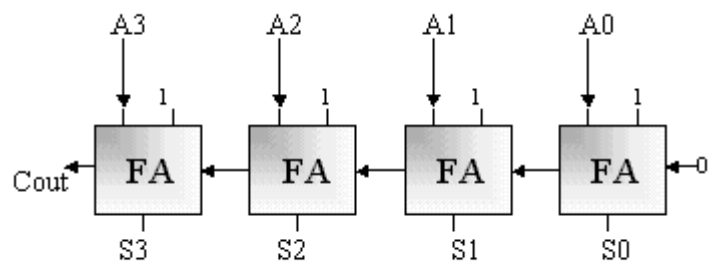

Question 4-14:

 


Question 4-15:

 


Question 4-16:

Building a combinational circuit capable of selecting and generating any of the 16 logic functions in table 4-5?

	F_i	$S_3 S_2 S_1 S_0$
0	$F_0 = 0$	0000
1	$F_1 = xy$	0001
2	$F_2 = xy'$	0010
3	$F_3 = x$	0011
4	$F_4 = x'y$	0100
5	$F_5 = y$	0101
6	$F_6 = x \text{ XOR } y$	0110
7	$F_7 = x + y$	0111
8	$F_8 = (x + y)'$	1000
9	$F_9 = (x \text{ XOR } y)'$	1001
10	$F_{10} = y'$	1010
11	$F_{11} = x + y'$	1011
12	$F_{12} = x'$	1100
13	$F_{13} = x' + y$	1101
14	$F_{14} = (xy)'$	1110
15	$F_{15} = 1$	1111

 

Question 4-17:

 

Question 4-18:

A = 1101 1001 (Note: A⁺ means the new value of Register A)

- a) A⁺ = 0110 1101 → B = 1011 0100 And the Logic Operation is **XOR**
- b) A⁺ = 1111 1101 → B = 1111 1101, And the Logic Operation is **OR**

Question 4-19:

Initially:

AR = 11110010, BR = 11111111, CR = 10111001, DR = 11101010

Determine the values of these registers after the execution of the following micro operations:

Micro operation	AR	BR	CR	DR
Initially	1111 0010	1111 1111	1011 1001	1110 1010
AR ← AR + BR	1111 0001	1111 1111	1011 1001	1110 1010
CR ← CR AND DR, BR ← BR + 1	1111 0001	0000 0000	1010 1000	1110 1010
AR ← AR - CR	0100 1001	0000 0000	1010 1000	1110 1010

Question 4-20:

Initially R = 1001 1100, which is -100 in Decimal.

Microoperation	R	Decimal value of R	Overflow
R \leftarrow ashr R	1100 1110	-50	No
R \leftarrow ashl R	0011 1000	+56	Yes

Question 4-21

Microoperation	R
Initially	1101 1101
R \leftarrow shl R	1011 1010
R \leftarrow cir R	0101 1101
R \leftarrow shr R	0010 1110
R \leftarrow cil R	0101 1100

Question 4-22:

What's the output H in Fig 4-12 if A is 1001, S=1, $I_R = 1$ and $I_L = 0$?

The value of H would be : $A_1 A_2 A_3 I_L = 0010$

Question 4-23:

What is wrong in the following?

- a. xT: AR \leftarrow (AR)', AR \leftarrow 0

The two microoperations -Compliment and Clear - are supposed to be done @ the same time on the same register, this is wrong coz these microoperations can't be implemented on the same register @ the same time.

- b. yT: R1 \leftarrow R2, R1 \leftarrow R3

These microoperations make no sense; coz two values are to be loaded into the same register at the same time.

- c. zT: PC \leftarrow AR, PC \leftarrow PC + 1

This statement is ambiguous; it doesn't determine what to be loaded into PC, the value of AR or incrementing PC, these are two conflicting microoperations that can't be implemented on the same register at the same time.